 


# CSL7070: Computer Architecture


## Lecture 9, 10<sup>th</sup> March 2023

Dip Sankar Banerjee




*Indian Institute of Technology, Jodhpur*  
*January-April 2023*

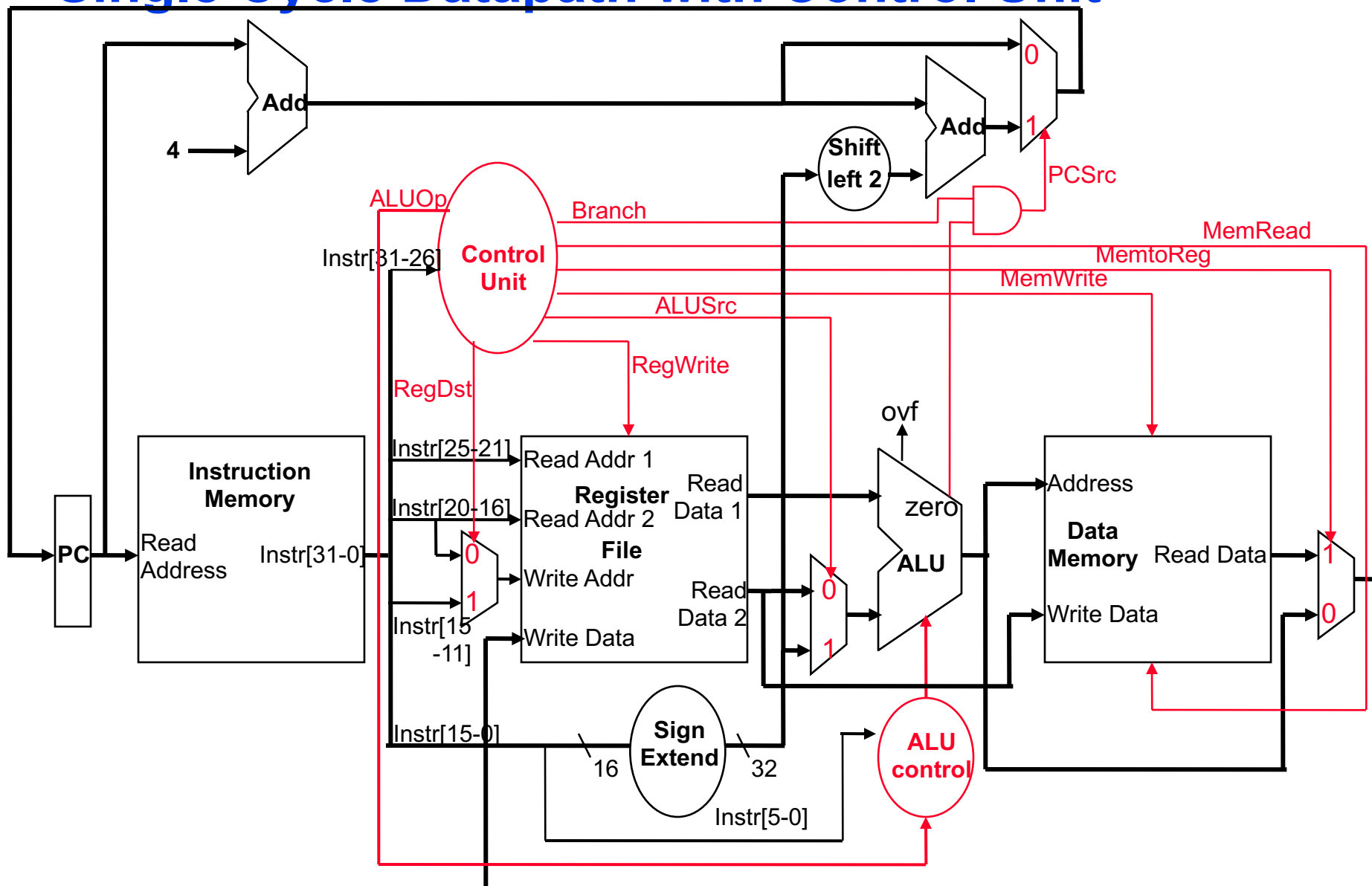
# Single Cycle Datapath with Control Unit




# R-type Instruction Data/Control Flow

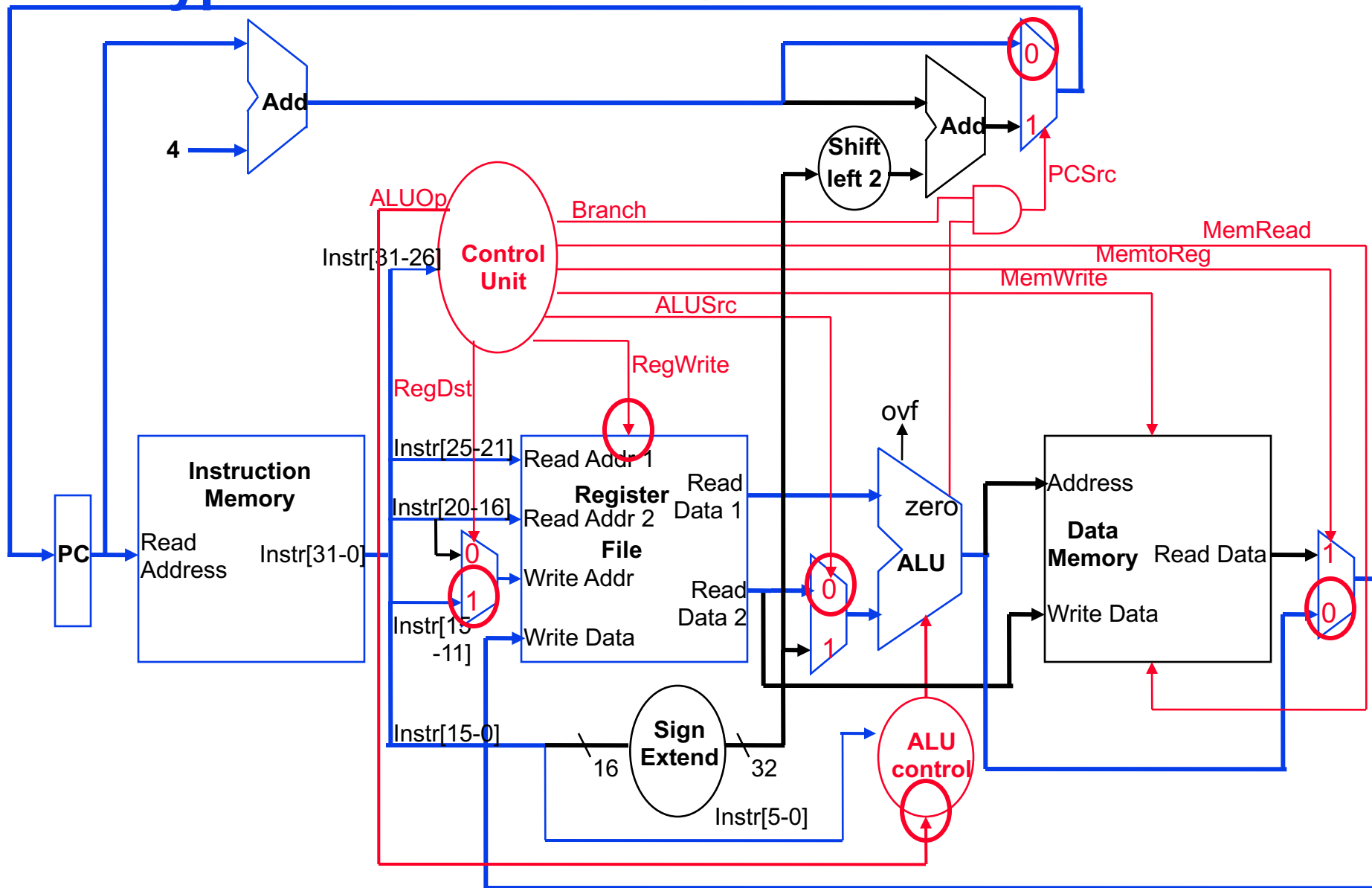

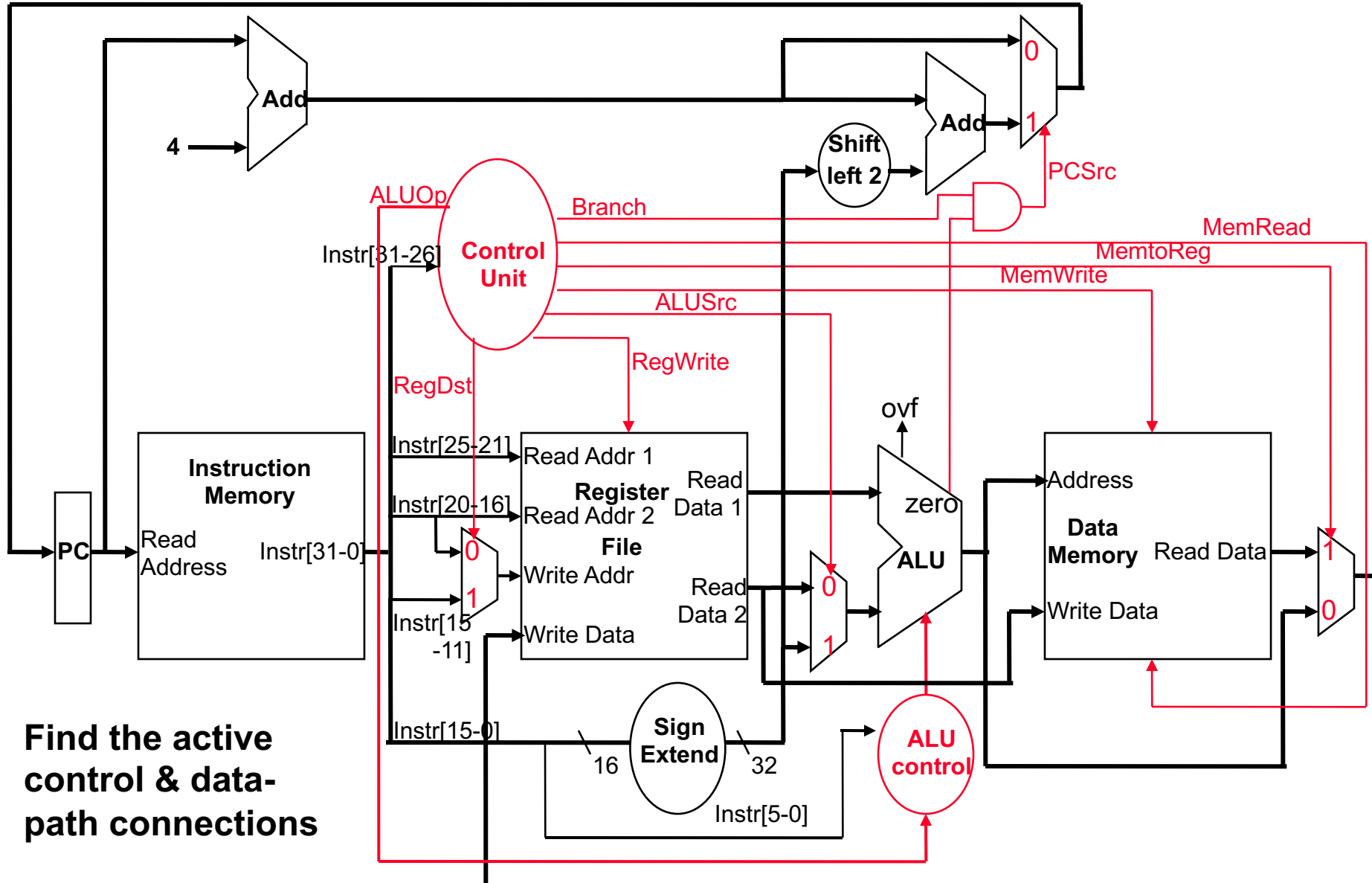
# Load Word Instruction Data/Control Flow



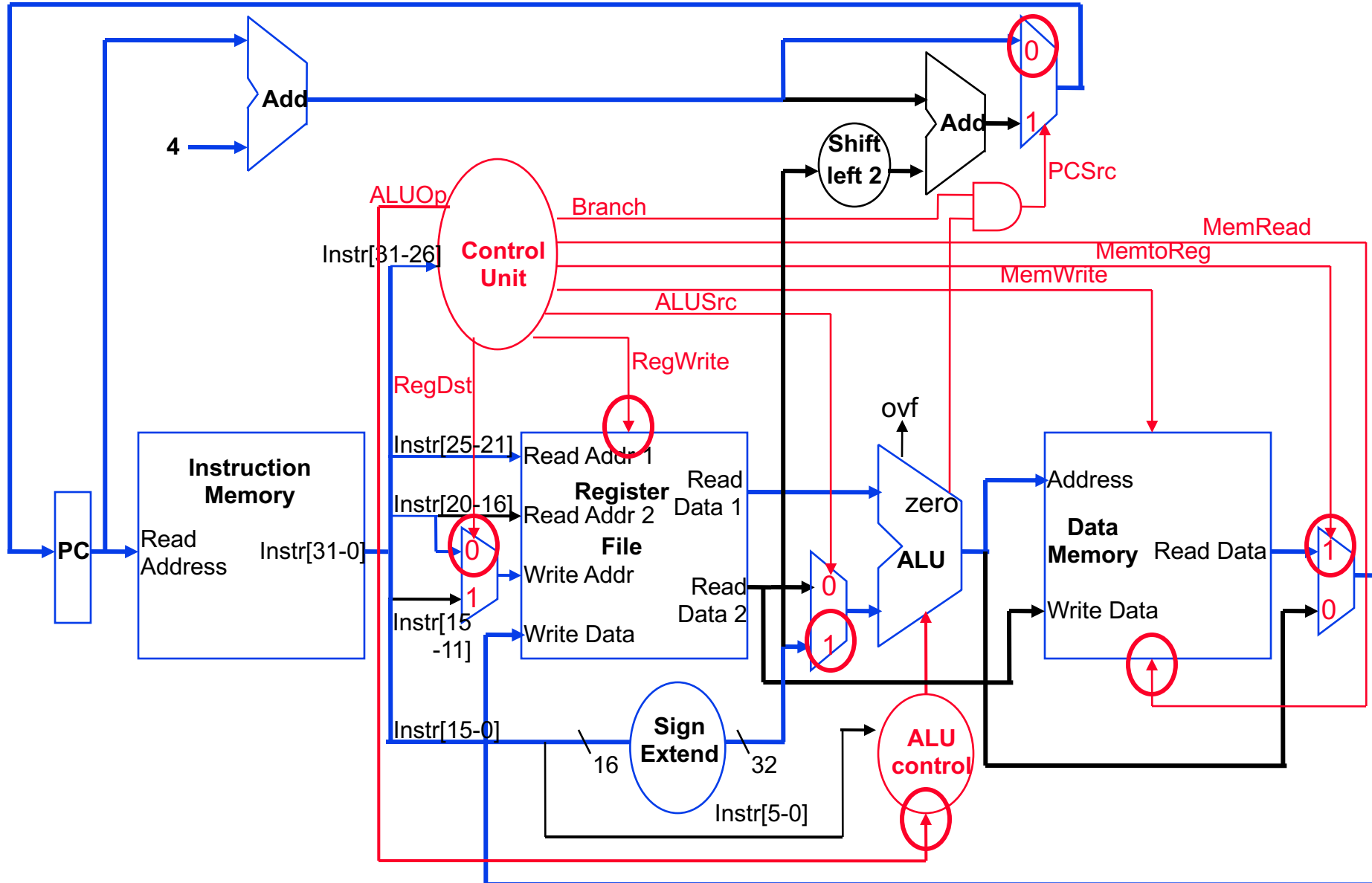
# Load Word Instruction Data/Control Flow




# Branch Instruction Data/Control Flow

 

# Branch Instruction Data/Control Flow

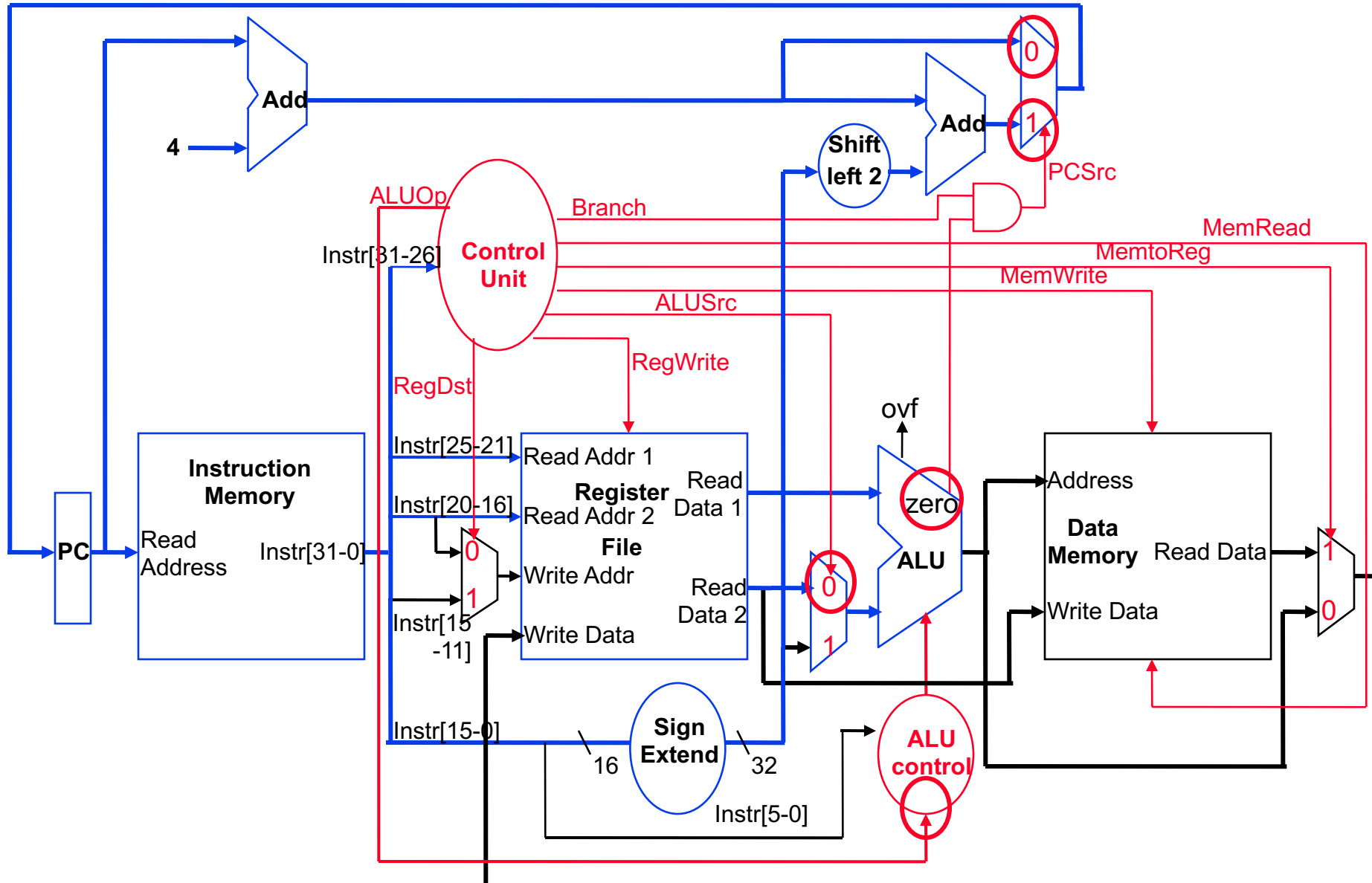

# Adding the Jump Operation

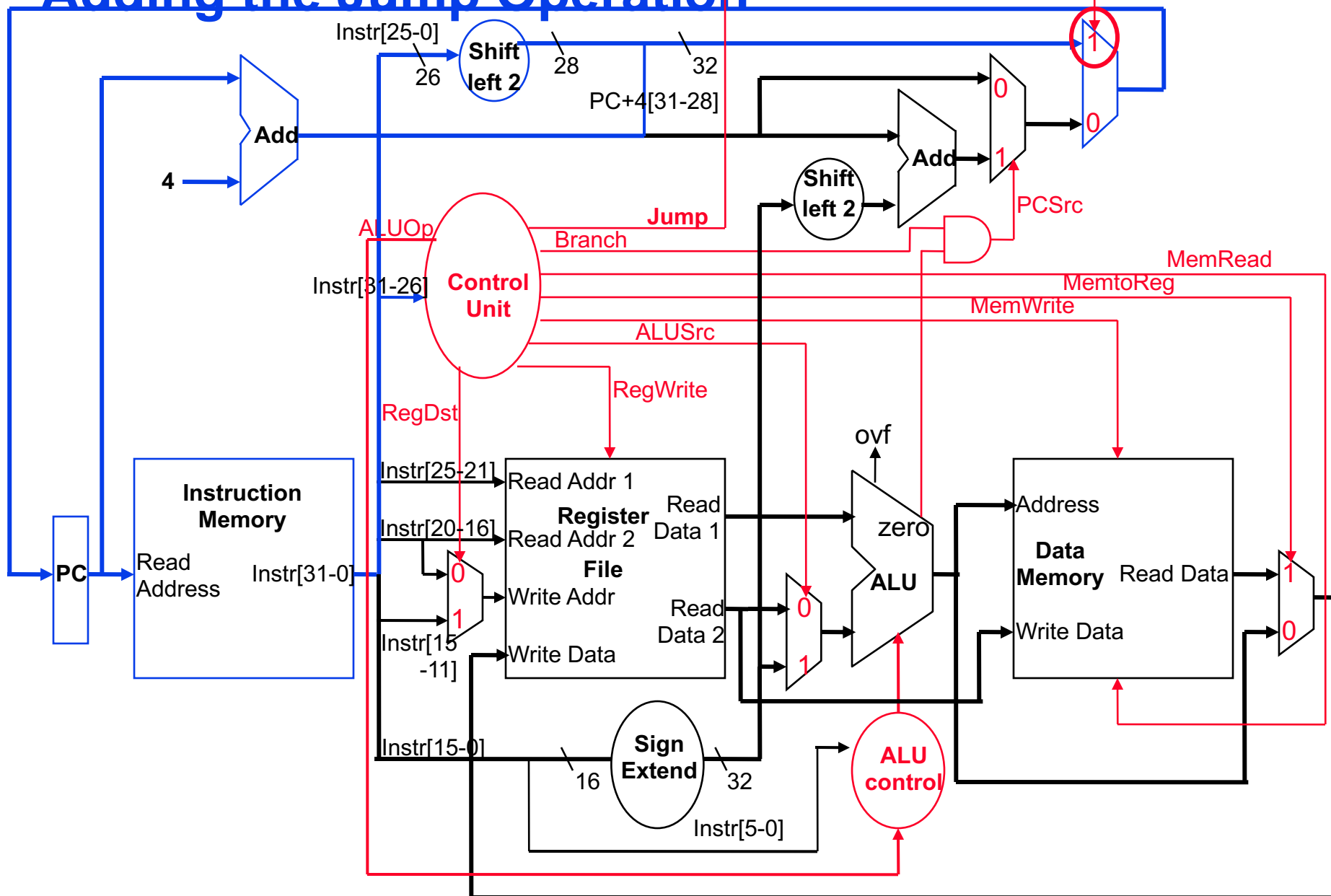



## Instruction Times (Critical Paths)

❑ What is the clock cycle time (assuming negligible delays for muxes, control unit, sign extend, PC access, shift left 2, wires, setup and hold times) but with:

- Instruction and Data Memory (200 ps)
- ALU and adders (200 ps)
- Register File access (reads or writes) (100 ps)

| Instr. | I Mem | Reg Rd | ALU Op | D Mem | Reg Wr | Total |
|--------|-------|--------|--------|-------|--------|-------|
| R-type |       |        |        |       |        |       |
| load   |       |        |        |       |        |       |
| store  |       |        |        |       |        |       |
| beq    |       |        |        |       |        |       |
| jump   |       |        |        |       |        |       |

## Instruction Critical Paths


❑ What is the clock cycle time (assuming negligible delays for muxes, control unit, sign extend, PC access, shift left 2, wires, setup and hold times) but with:

- Instruction and Data Memory (200 ps)
- ALU and adders (200 ps)
- Register File access (reads or writes) (100 ps)

| Instr. | I Mem | Reg Rd | ALU Op | D Mem | Reg Wr | Total |
|--------|-------|--------|--------|-------|--------|-------|
| R-type | 200   | 100    | 200    |       | 100    | 600   |
| load   | 200   | 100    | 200    | 200   | 100    | 800   |
| store  | 200   | 100    | 200    | 200   |        | 700   |
| beq    | 200   | 100    | 200    |       |        | 500   |
| jump   | 200   |        |        |       |        | 200   |
 
# Single Cycle Disadvantages & Advantages

- ❑ Uses the clock cycle inefficiently – the clock cycle must be timed to accommodate the **slowest** instruction
  - especially problematic for more complex instructions like floating point multiply



- ❑ May be wasteful of area since some functional units (e.g., adders) must be duplicated since they can not be shared during a clock cycle


but

- ❑ Is simple and easy to understand

## How Can We Make It Faster?

- ❑ Start fetching and executing the next instruction before the current one has completed
  - **Pipelining** – all modern processors are pipelined for performance
  - Remember *the* performance equation:  
$$\text{CPU time} = \text{CPI} * \text{CC} * \text{IC}$$
- ❑ Under *ideal* conditions and with a large number of instructions, the speedup from pipelining is approximately equal to the number of pipe stages
  - A five stage pipeline is nearly five times faster because the CC is nearly five times faster
- ❑ Fetch (and execute) more than one instruction at a time
  - Superscalar processing – stay tuned

# The Five Stages of Load Instruction

 


- ❑ IFetch: Instruction Fetch and Update PC
- ❑ Dec: Registers Fetch and Instruction Decode
- ❑ Exec: Execute R-type; calculate memory address
- ❑ Mem: Read/write the data from/to the Data Memory
- ❑ WB: Write the result data into the register file
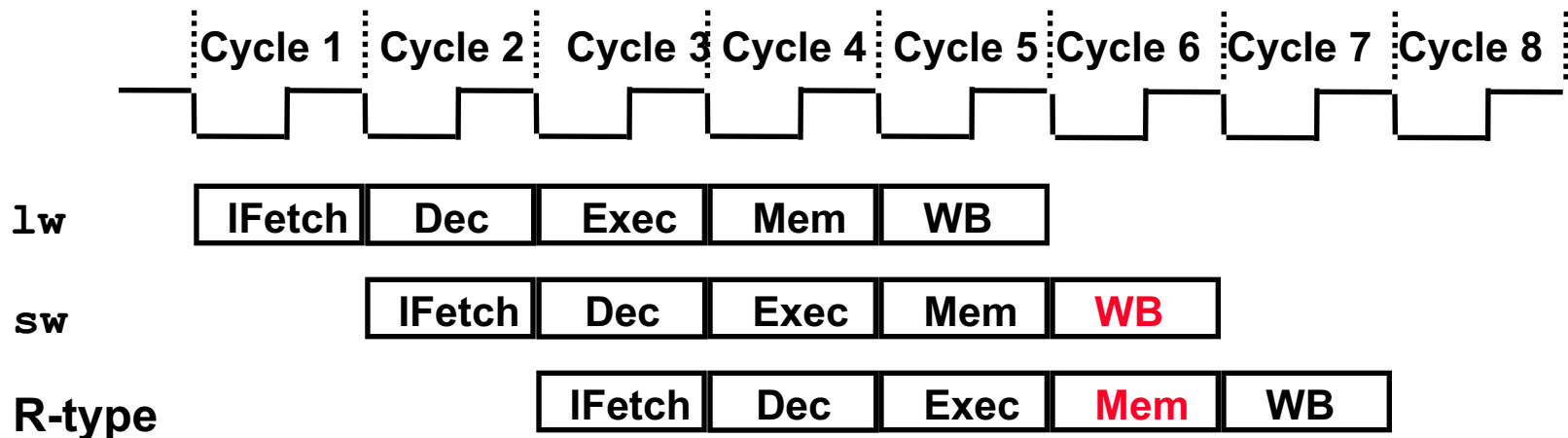
# A Pipelined RISC Processor

❑ Start the **next** instruction before the current one has completed


- improves **throughput** - total amount of work done in a given time
- instruction **latency** (execution time, delay time, response time - time from the start of an instruction to its completion) is *not* reduced




- clock cycle (pipeline stage time) is limited by the **slowest** stage
  - for some stages don't need the whole clock cycle (e.g., WB)
  - for some instructions, some stages are **wasted** cycles (i.e., nothing is done during that cycle for that instruction)
 
# Single Cycle versus Pipeline

Single Cycle Implementation (CC = 800 ps):



Pipeline Implementation (CC = 200 ps):

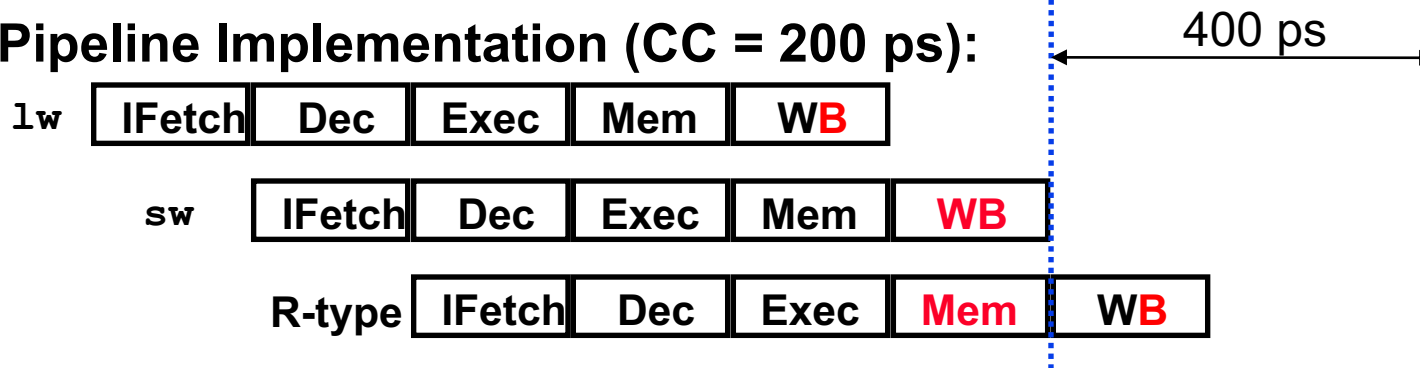

- ☐ To complete an entire instruction in the pipelined case takes 1000 ps (as compared to 800 ps for the single cycle case). Why ?
- ☐ How long does each take to complete 1,000,000 adds ?

# Pipelining the RISC ISA


## □ What makes it easy

- all instructions are the same length (32 bits)
  - can fetch in the 1<sup>st</sup> stage and decode in the 2<sup>nd</sup> stage
- few instruction formats (only 3) with **symmetry** across formats
  - can begin reading register file in 2<sup>nd</sup> stage
- memory operations occur only in loads and stores
  - can use the execute stage to calculate memory addresses
- each instruction writes at most one result (i.e., changes the machine state) and does it in the last few pipeline stages (MEM or WB)
- operands must be aligned in memory so a single data transfer takes only one data memory access


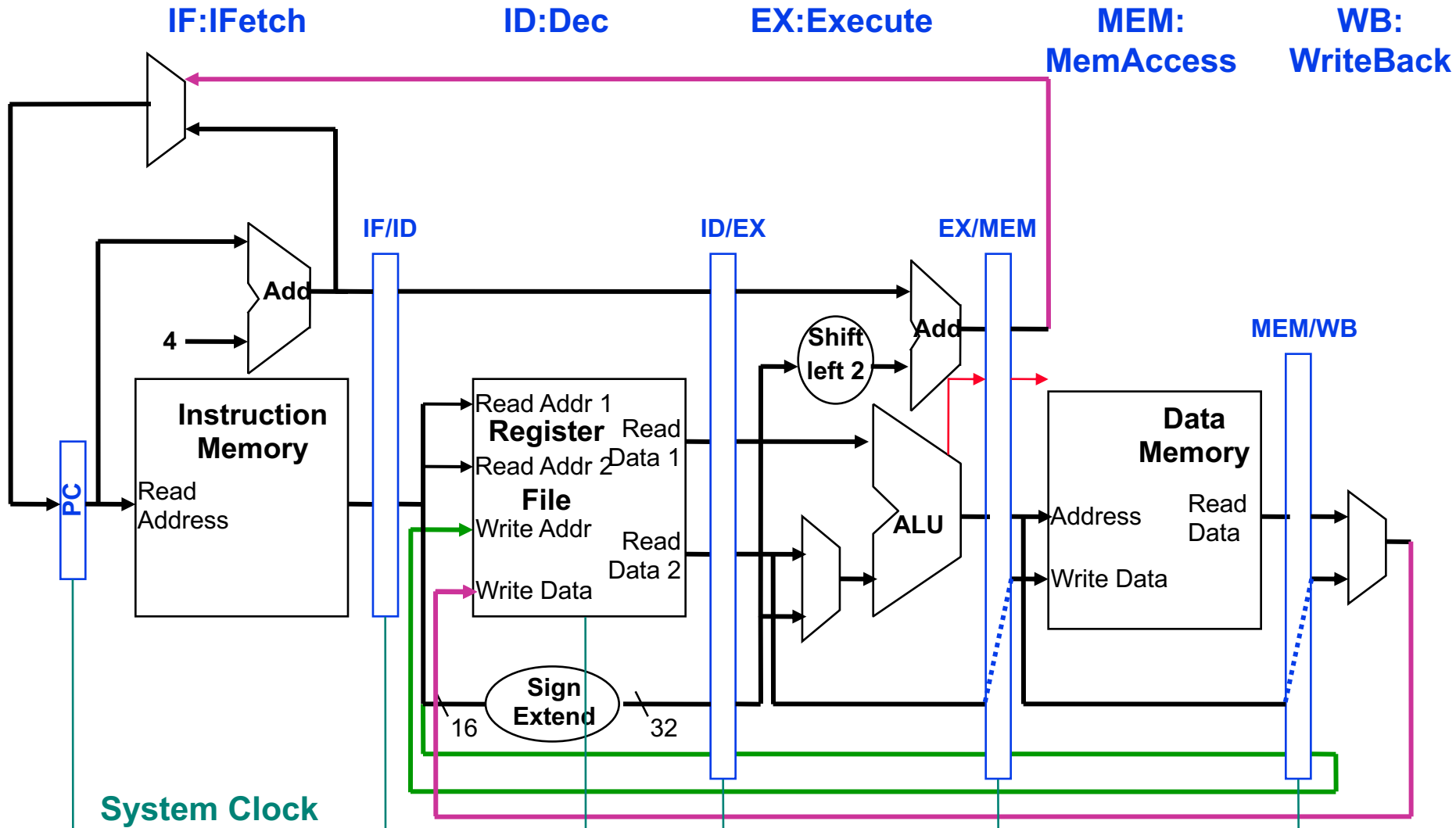
# RISC Pipeline Datapath Additions/Mods


❑ State registers between each pipeline stage to **isolate** them


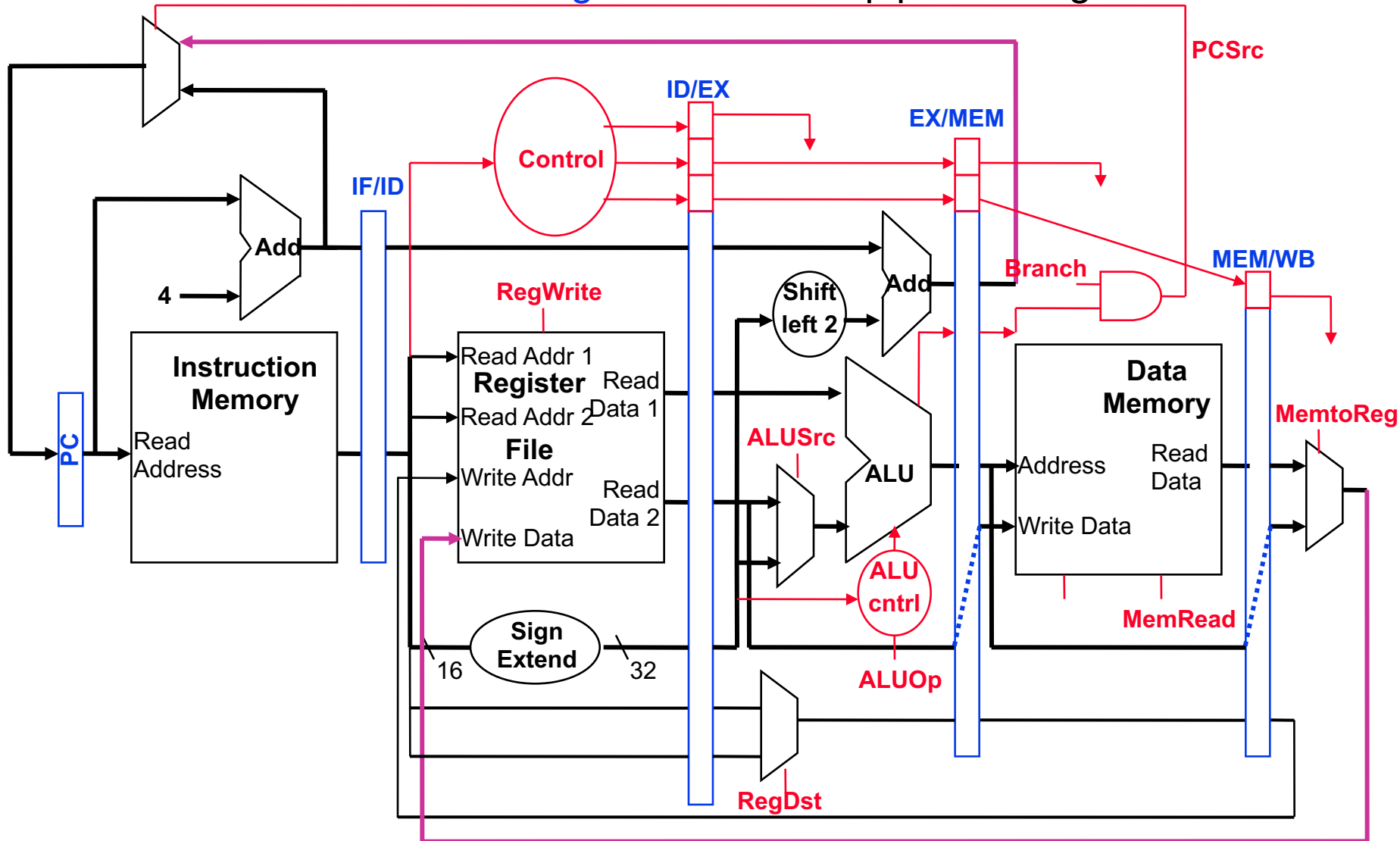
# RISC Pipeline Control Path Modifications

❑ All control signals can be determined during Decode

● and held in the **state registers** between pipeline stages




# Pipeline Control

- ❑ IF Stage: read Instr Memory (always asserted) and write PC (on System Clock)
- ❑ ID Stage: no optional control signals to set

|     | EX Stage |         |         |         | MEM Stage |          |           | WB Stage  |           |
|-----|----------|---------|---------|---------|-----------|----------|-----------|-----------|-----------|
|     | Reg Dst  | ALU Op1 | ALU Op0 | ALU Src | Brch      | Mem Read | Mem Write | Reg Write | Mem toReg |
| R   | 1        | 1       | 0       | 0       | 0         | 0        | 0         | 1         | 0         |
| lw  | 0        | 0       | 0       | 1       | 0         | 1        | 0         | 1         | 1         |
| sw  | X        | 0       | 0       | 1       | 0         | 0        | 1         | 0         | X         |
| beq | X        | 0       | 1       | 0       | 1         | 0        | 0         | 0         | X         |


# Graphically Representing RISC Pipeline

 

- ❑ Can help with answering questions like:
- How many cycles does it take to execute this code?
  - What is the ALU doing during cycle 4?
  - Is there a hazard, why does it occur, and how can it be fixed?

# Why Pipeline? For Performance!

Time (clock cycles)

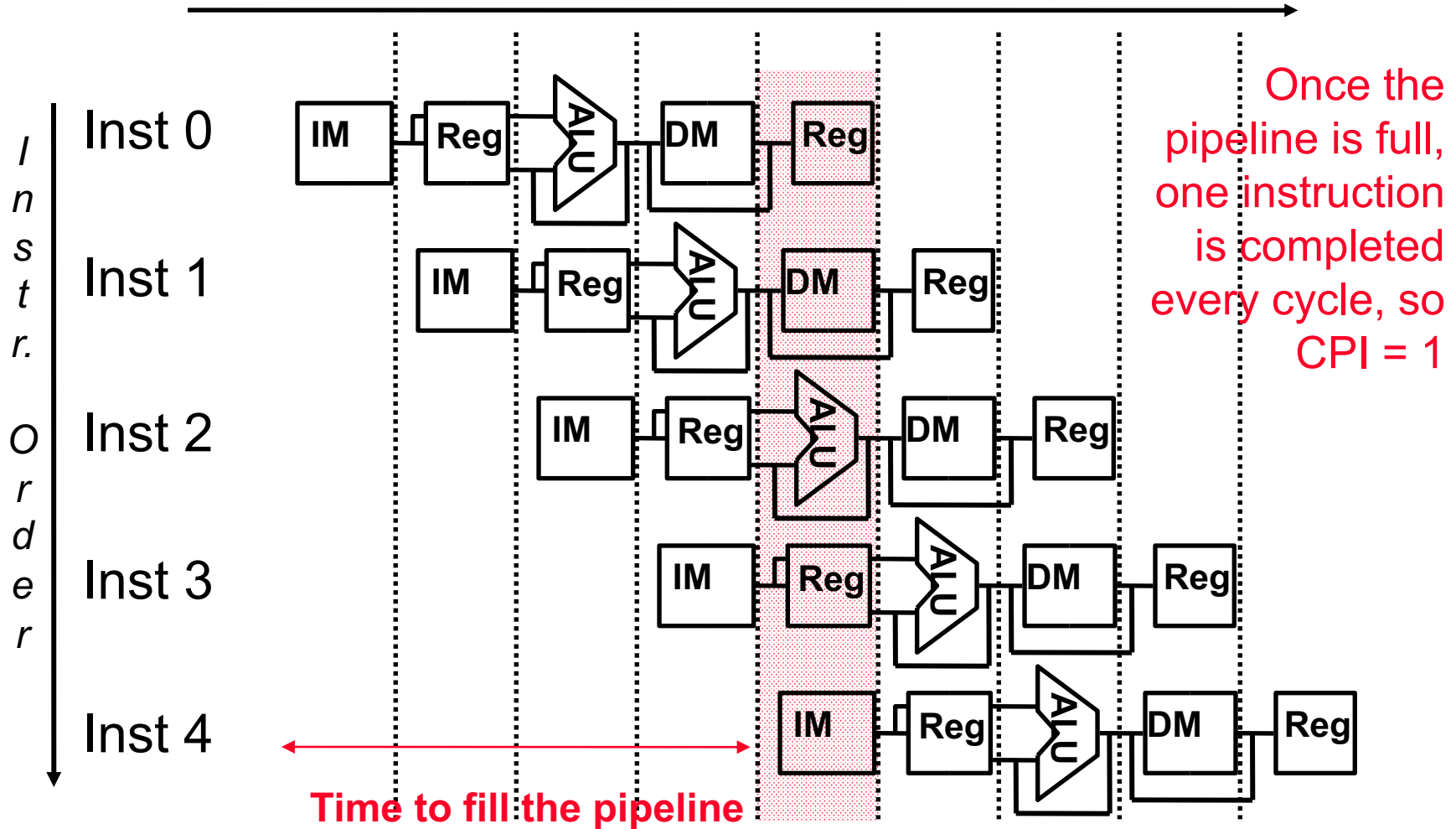

# Can Pipelining Get Us Into Trouble?

## ☐ Yes: Pipeline Hazards


- **structural hazards**: attempt to use the same resource by two different instructions at the same time
- **data hazards**: attempt to use data before it is ready
  - An instruction's source operand(s) are produced by a prior instruction still in the pipeline
- **control hazards**: attempt to make a decision about program control flow before the condition has been evaluated and the new PC target address calculated
  - branch and jump instructions, exceptions

## ☐ Can usually resolve hazards by waiting

- pipeline control must **detect** the hazard
- and take action to **resolve** hazards

# A Single Memory Would Be a Structural Hazard


Time (clock cycles)

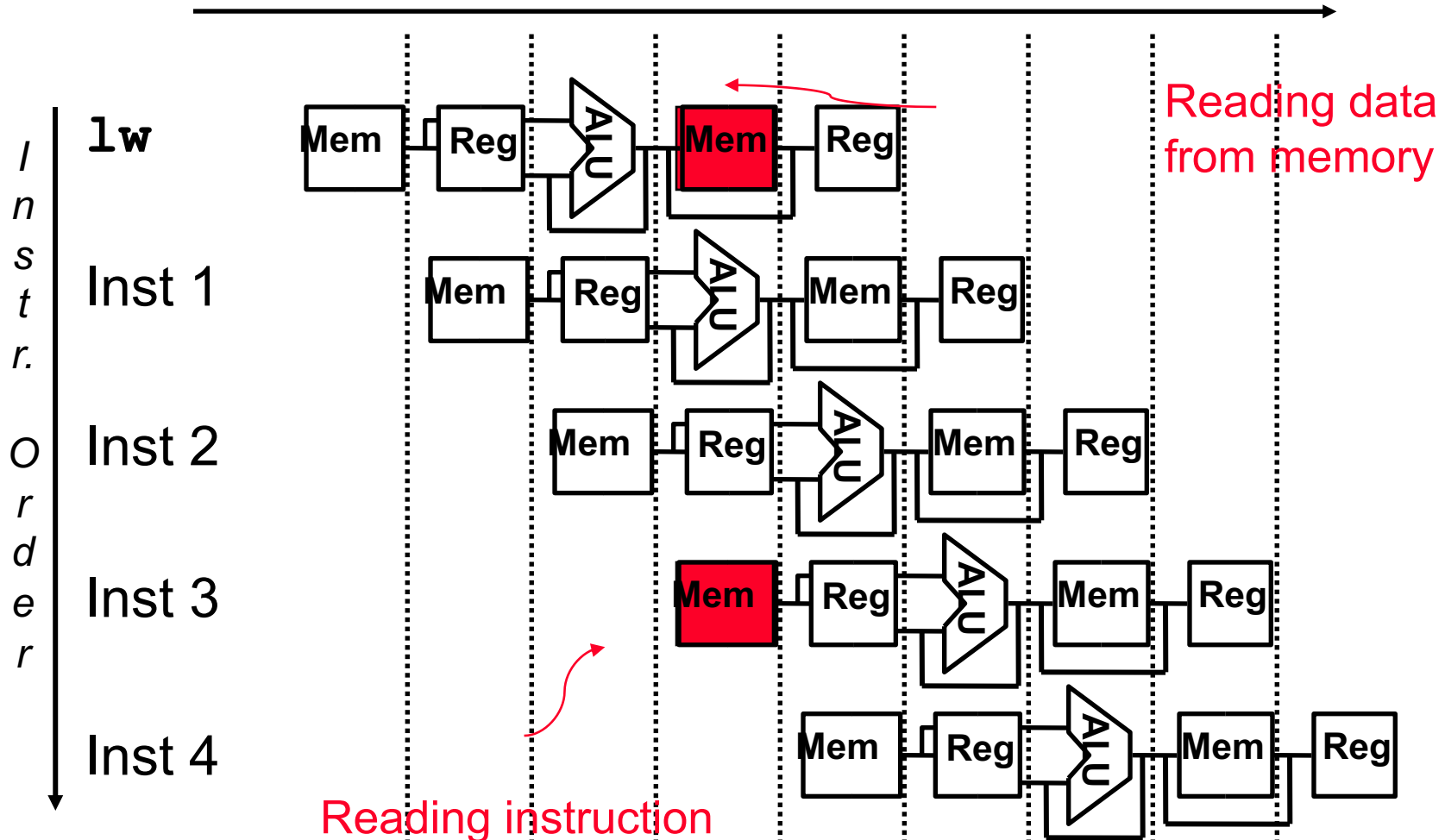

□ Fix with separate instr and data memories (I\$ and D\$)

# How About Register File Access?


Time (clock cycles)

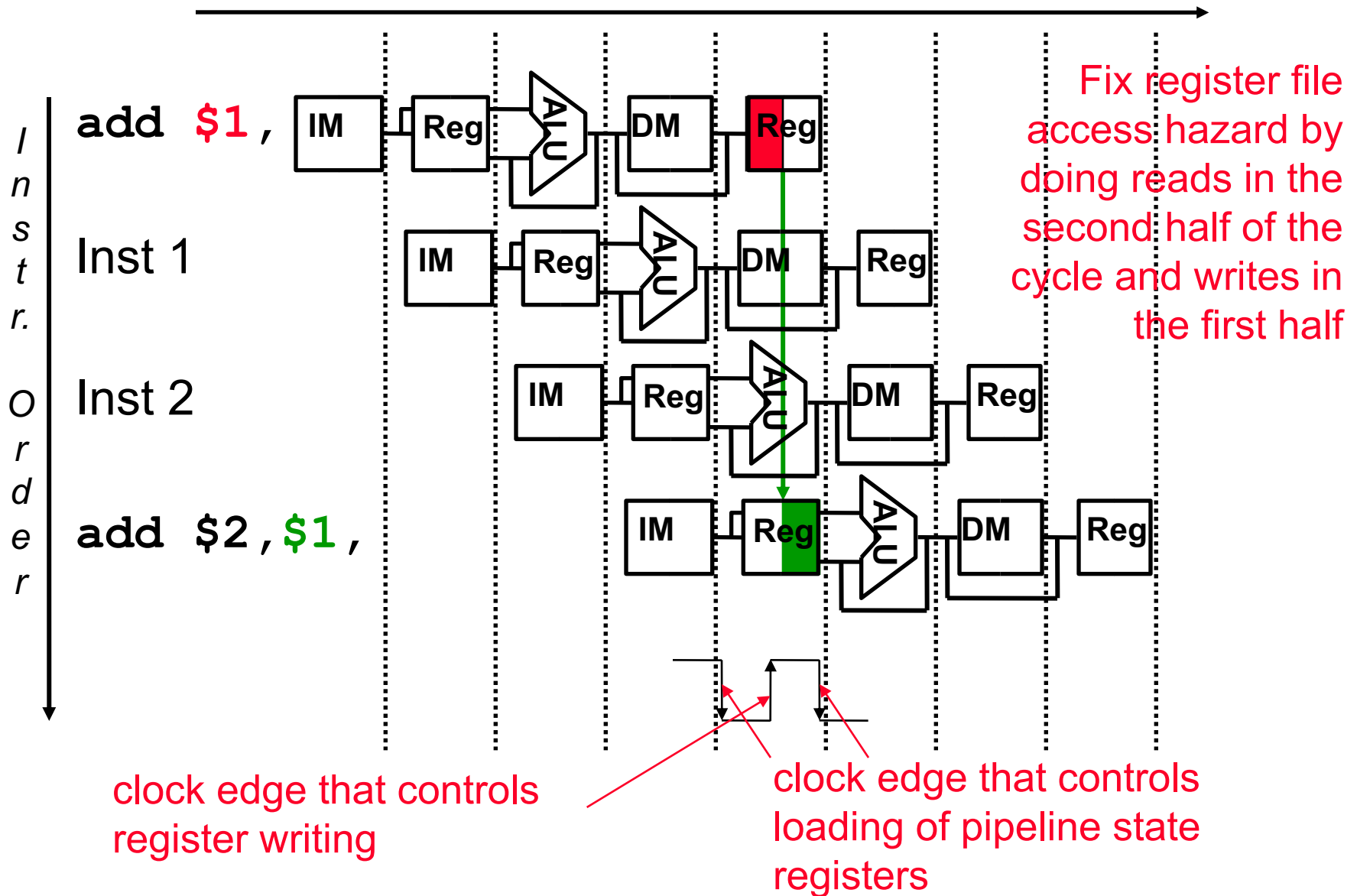


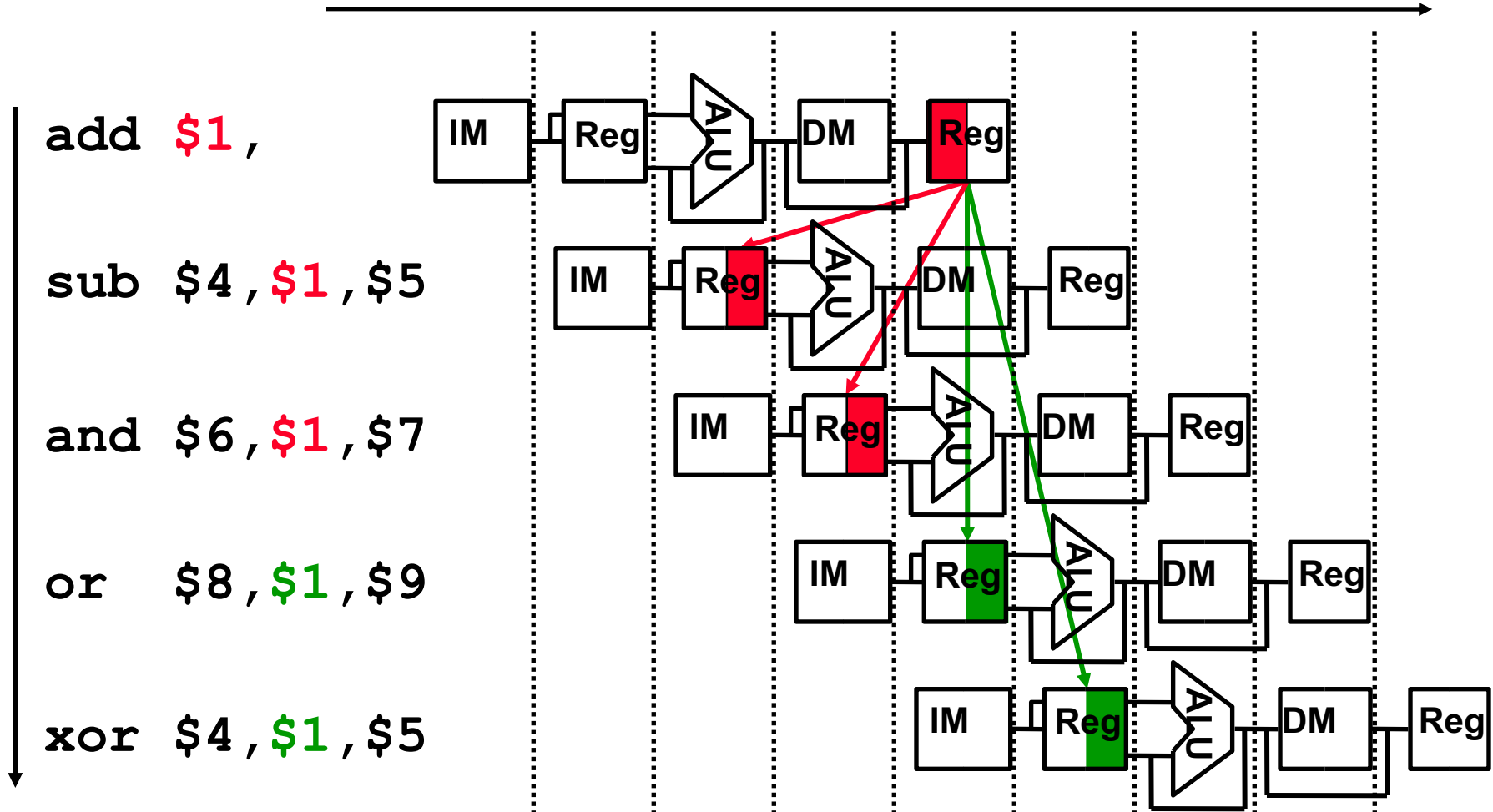
# Register Usage Can Cause Data Hazards


❑ Dependencies backward in time cause **hazards**



❑ Read after write data hazard (RAW in the code)
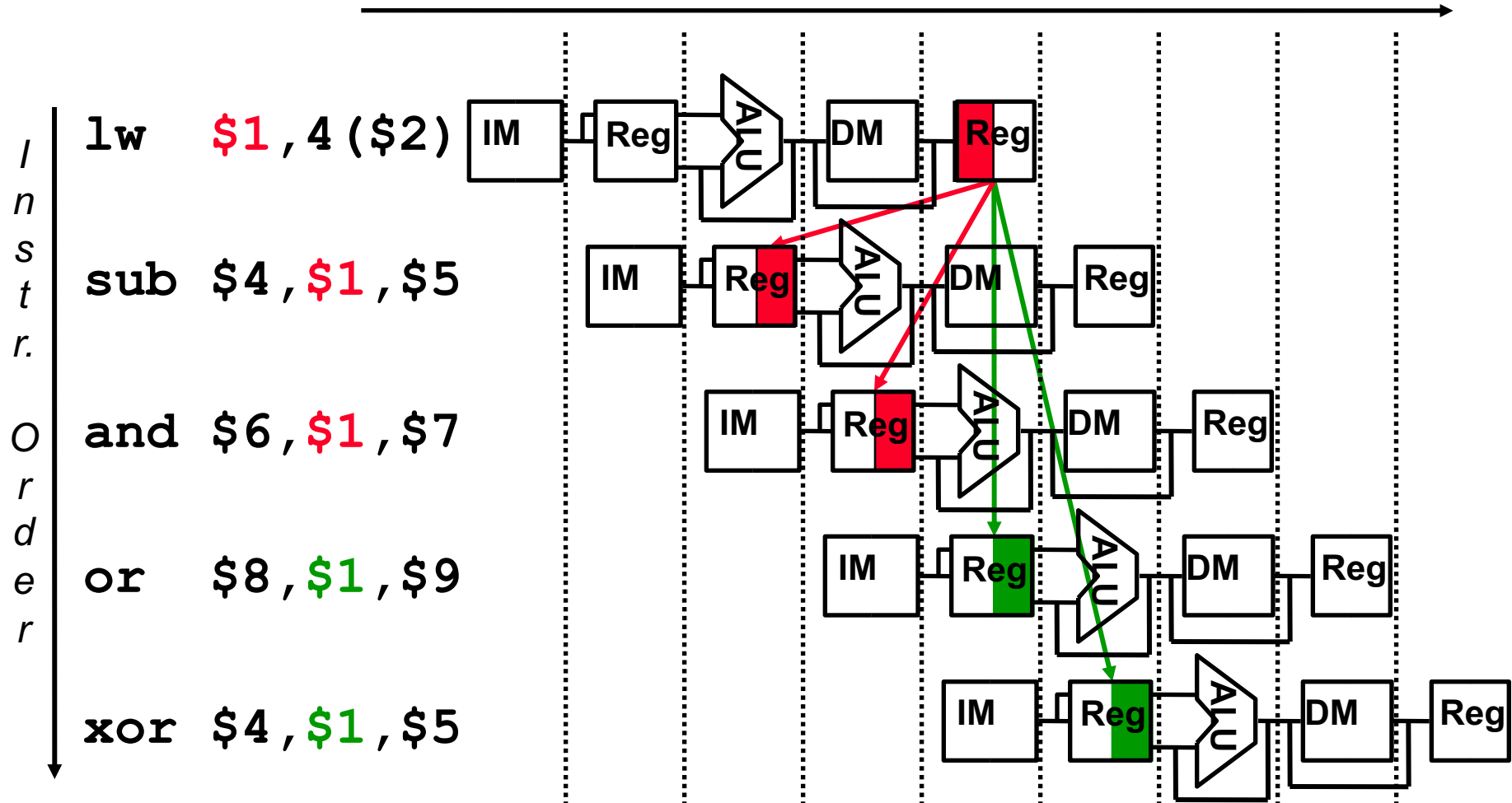
# Loads Can Cause Data Hazards


Dependencies backward in time cause hazards



Load-use data hazard
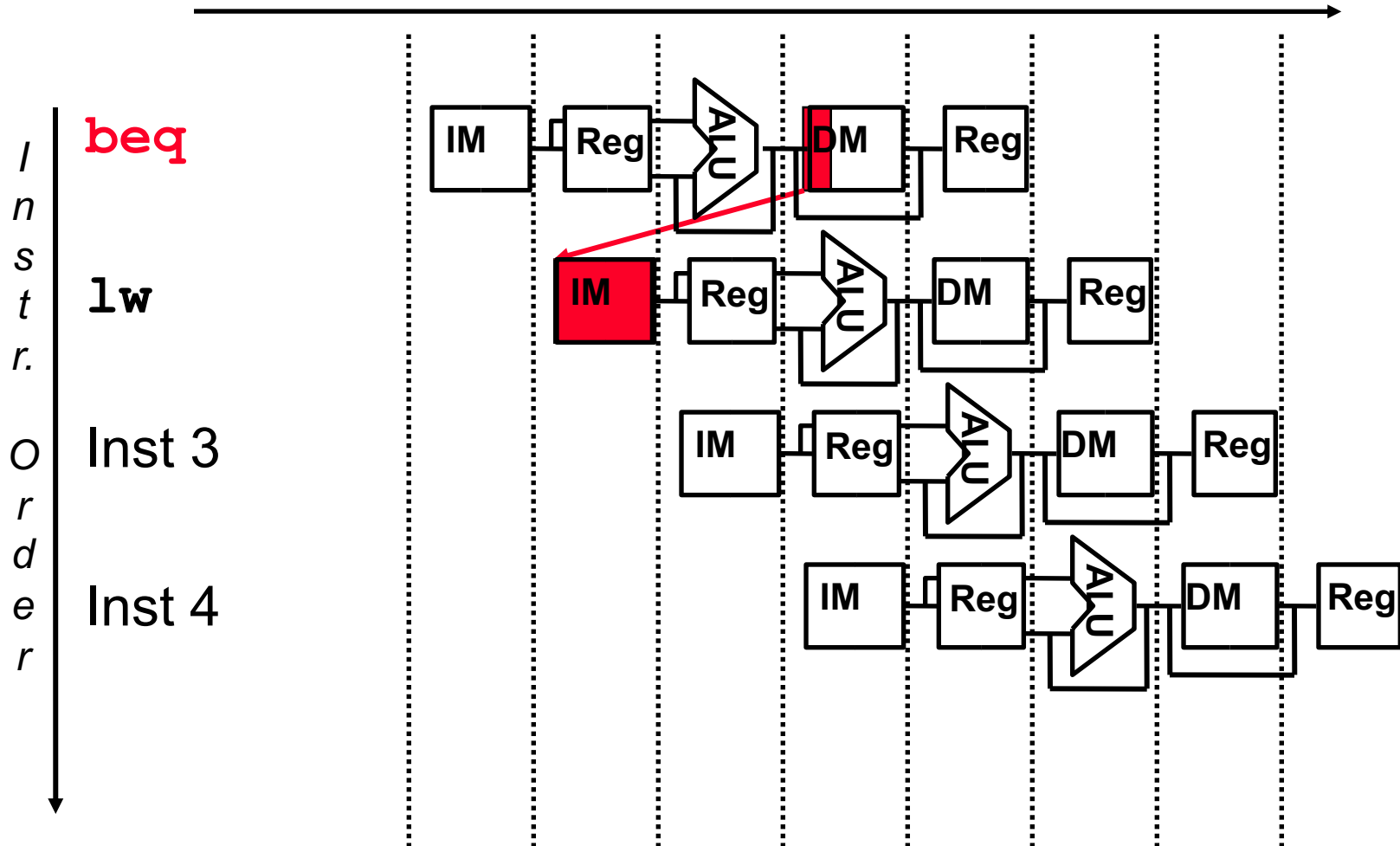
# Branch Instructions Cause Control Hazards


□ Dependencies backward in time cause **hazards**


 
## Other Pipeline Structures Are Possible


❑ What about the (slow) multiply operation?

- Make the clock twice as slow or ...
- let it take two cycles (since it doesn't use the DM stage)




❑ What if the data memory access is twice as slow as the instruction memory?

 - make the clock twice as slow or ...
- let data memory access take two cycles (and keep the same clock rate)




# Other Sample Pipeline Alternatives

## ARM7

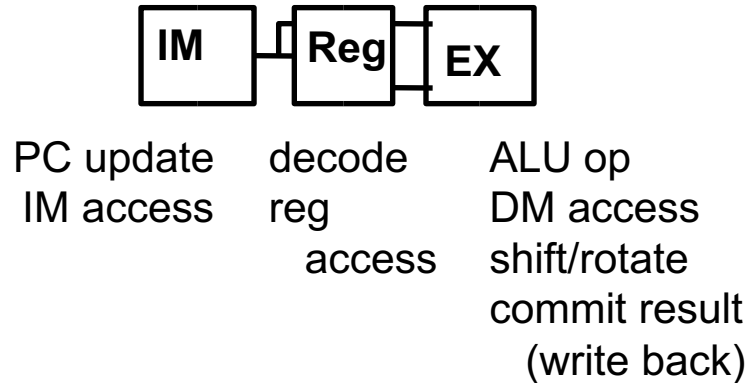

## XScale

 

# Summary

- ❑ All modern day processors use pipelining
- ❑ Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- ❑ Potential speedup: a CPI of 1 and fast a CC
- ❑ Pipeline rate limited by **slowest** pipeline stage
  - Unbalanced pipe stages makes for inefficiencies
  - The time to “**fill**” pipeline and time to “**drain**” it can impact speedup for deep pipelines and short code runs
- ❑ Must detect and resolve hazards
  - Stalling negatively affects CPI (makes CPI less than the ideal of 1)