

CSL7070: Computer Architecture

Lecture 7, 9th February 2022

Dip Sankar Banerjee



Indian Institute of Technology, Jodhpur
January-April 2022

Building a Datapath

- Datapath
 - Elements that process data and addresses in the CPU
 - Registers, ALUs, MUX's, memories, ...
- We will build a MIPS datapath incrementally
 - Refining the overview design

Instruction Fetch (IF) RTL

A language to
define hardware

- Common RTL operations

- Fetch instruction

Mem[PC] ;

Fetch instruction from memory


- Update program counter

- Sequential

PC <- PC + 4 ;

Calculate next address

Datapath: Instruction Fetch Unit

 

Add RTL

Add instruction

add rd, rs, rt

Mem[PC]; Fetch instruction from memory
R[rd] ← R[rs] + R[rt]; Add operation
PC ← PC + 4; Calculate next address

R-type
add t0, t1, t2
d s t

ISA
Assembly
ISA

sll
slli
srl
srl

Bits

6	5	5	5	5	6
OP=0	rs	rt	rd	sa	funct

first source register second source register result register shift amount function code (=32)

Sub RTL

- Sub instruction

sub rd, rs, rt

Mem[PC]; Fetch instruction from memory

R[rd] <- R[rs] - R[rt]; Sub operation

PC <- PC + 4; Calculate next address


Bits

6	5	5	5	5	6
OP=0	rs	rt	rd	sa	funct

first second result shift function
 source source register amount code
 register register (=34)

Datapath: Reg-Reg Operations

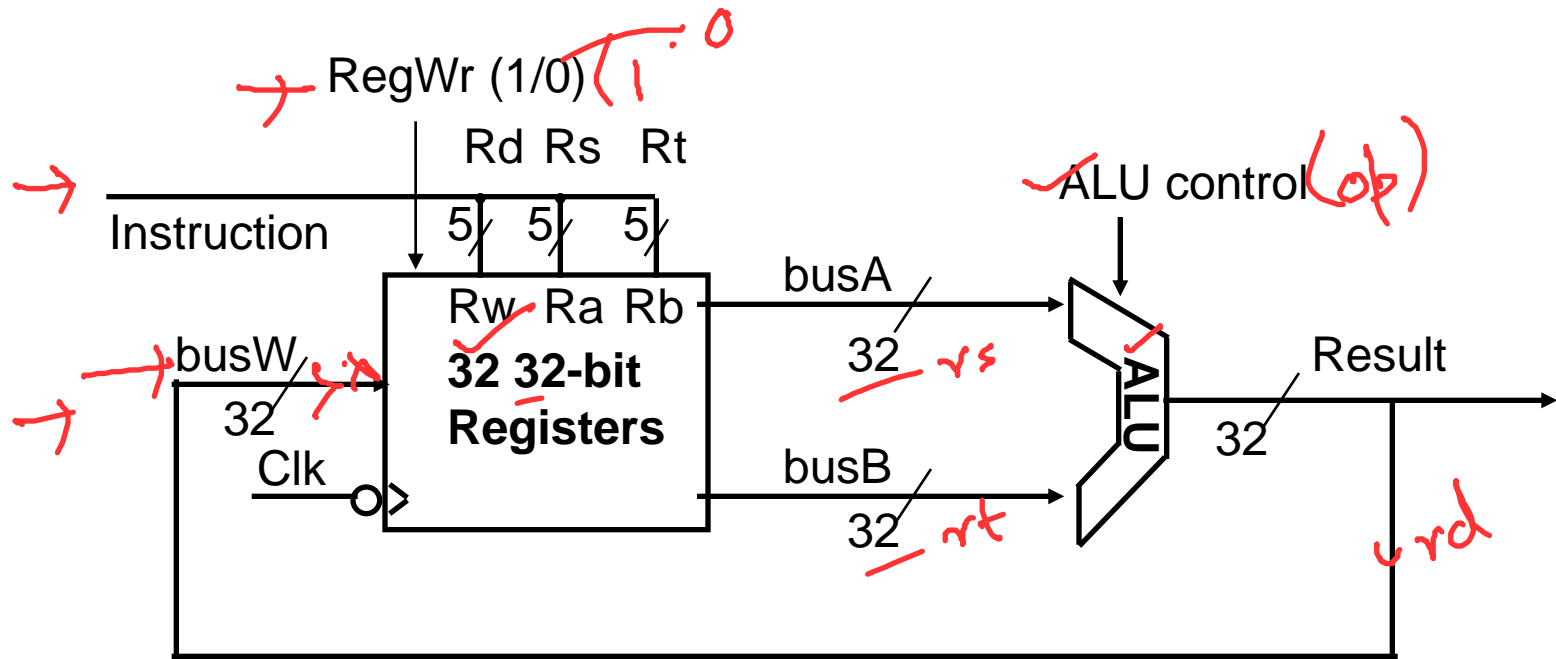- $R[rd] \leftarrow R[rs] \text{ op } R[rt];$
 - ALU control and RegWr coming from Control Unit, based on decoded instruction
 - Ra, Rb, and Rw from rs, rt, rd fields



OR Immediate RTL

• OR Immediate instruction

ori rt, rs, imm

Mem[PC];

Fetch instruction from memory

R[rt] <- R[rs] OR ZeroExt(imm);

OR operation with Zero-Extend

PC <- PC + 4;

Calculate next address

~~add~~ addi

-28 → 2⁸-1

2¹⁶

Bits

6

5

5

16

OP

rs

rt


imm

first source register
second register (dest)

immediate

Datapath: Immediate Ops

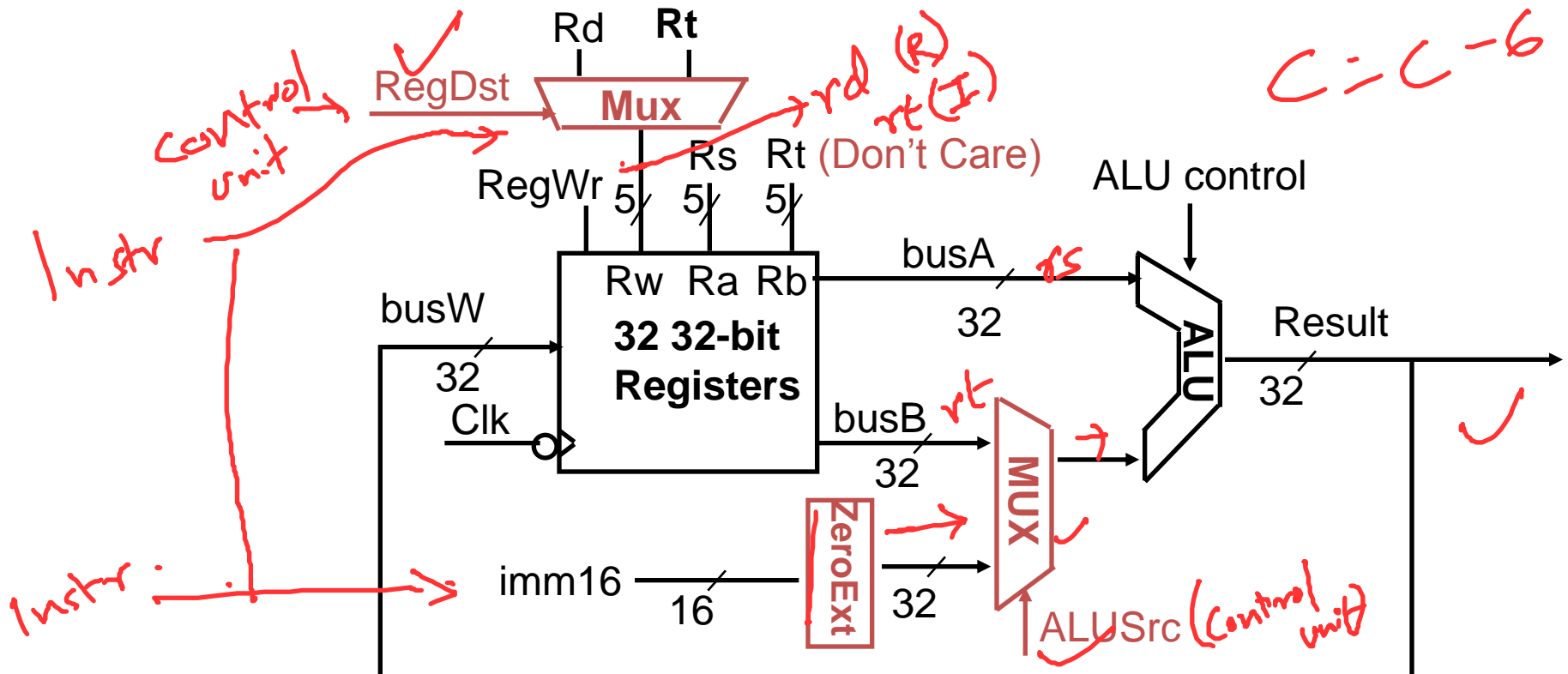- Rw set by MUX and ALU B set as busB or ZeroExt(imm)
- ALUSrc and RegDst set based on instruction



Load RTL

- Load instruction

`lw rt, rs, imm`

`Mem[PC];` Fetch instruction from memory
`Addr <- R[rs] + SignExt(imm);` Compute memory address
`R[rt] <- Mem[Addr];` Load data into register
`PC <- PC + 4;` Calculate next address

Bits

6

5

5

16

OP	rs	rt	imm
----	----	----	-----

first
 source
 register
 first
 source
 register


second
 register
 (dest)

immediate

Datapath: Load

sw rt, rs, #t(imm)

 - Extender handles sign vs. zero extension of immediate
- MUX selects between ALU result and Memory output



Store RTL

- Store instruction

`sw rt, rs, imm`

```
Mem[PC];           Fetch instruction from memory
Addr <- R[rs] + SignExt(imm); Compute memory addr
Mem[Addr] <- R[rt]; Load data into register
PC <- PC + 4;       Calculate next address
```

Bits

6

5

5

16


OP	rs	rt	imm
----	----	----	-----

first source register
second source register

immediate

Datapath: Store

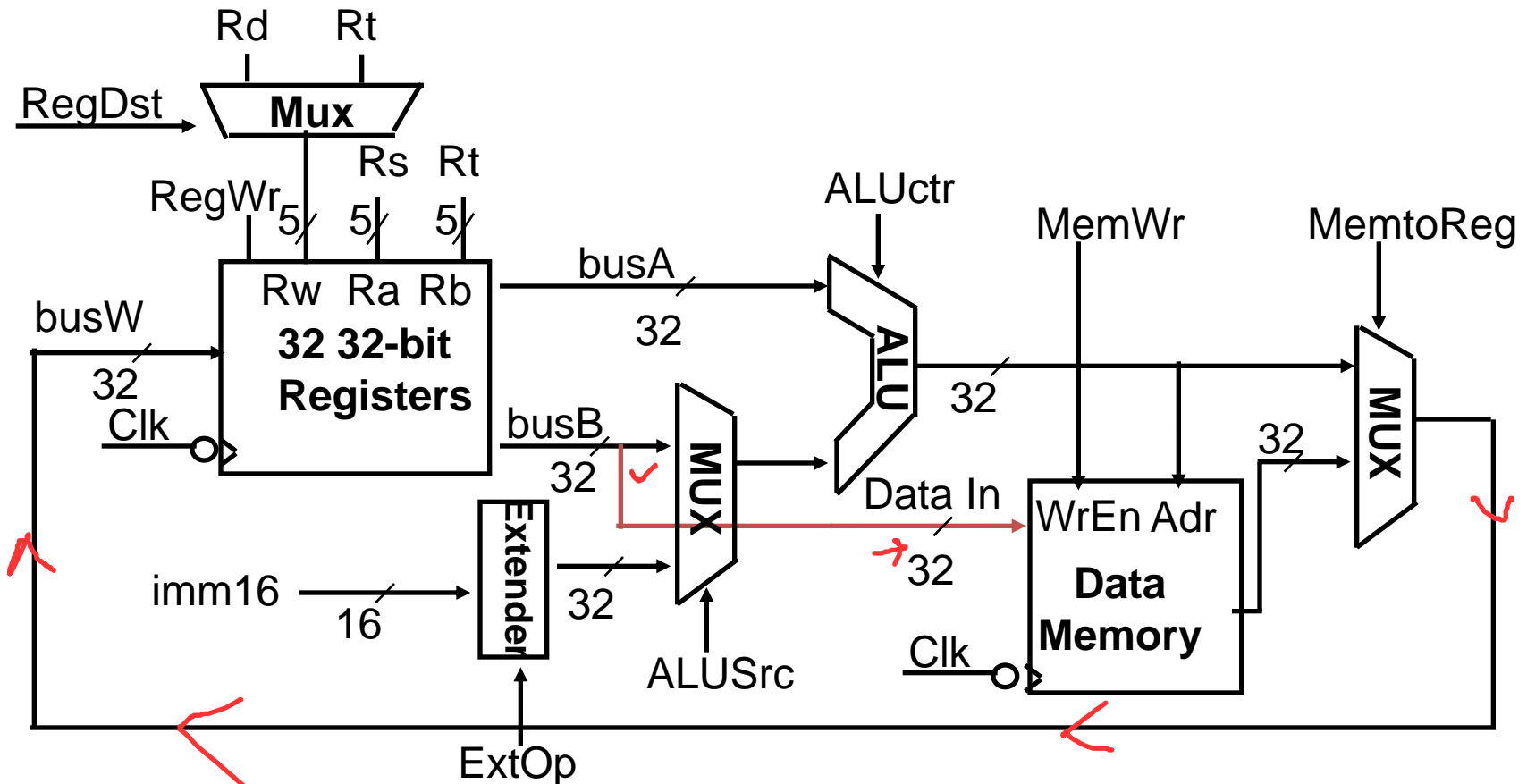- Register rt is passed on $busB$ into memory
- Memory address calculated just as in lw case



Branch RTL

- Branch instruction

beq rs, rt, imm

Mem[PC]; Fetch instruction from memory

Diff <- R[rs] - R[rt]; Calculate branch condition


if (Diff eq 0) Test if equal

PC <- PC + 4 +

SignExt(imm) * 4; Calculate PC Relative address

else

PC <- PC + 4; Calculate next address

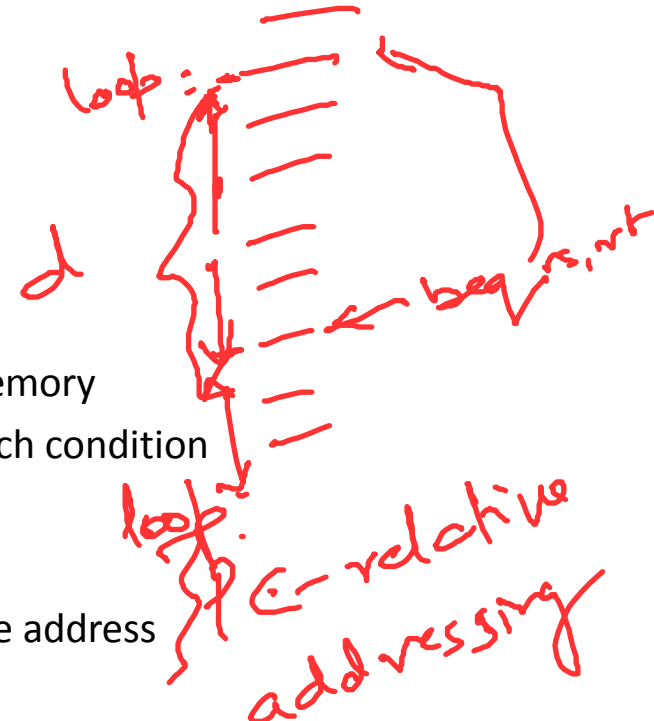

Bits

6

5

5

16

OP

rs

rt


imm

first
source

second
source

immediate

Datapath: Branch

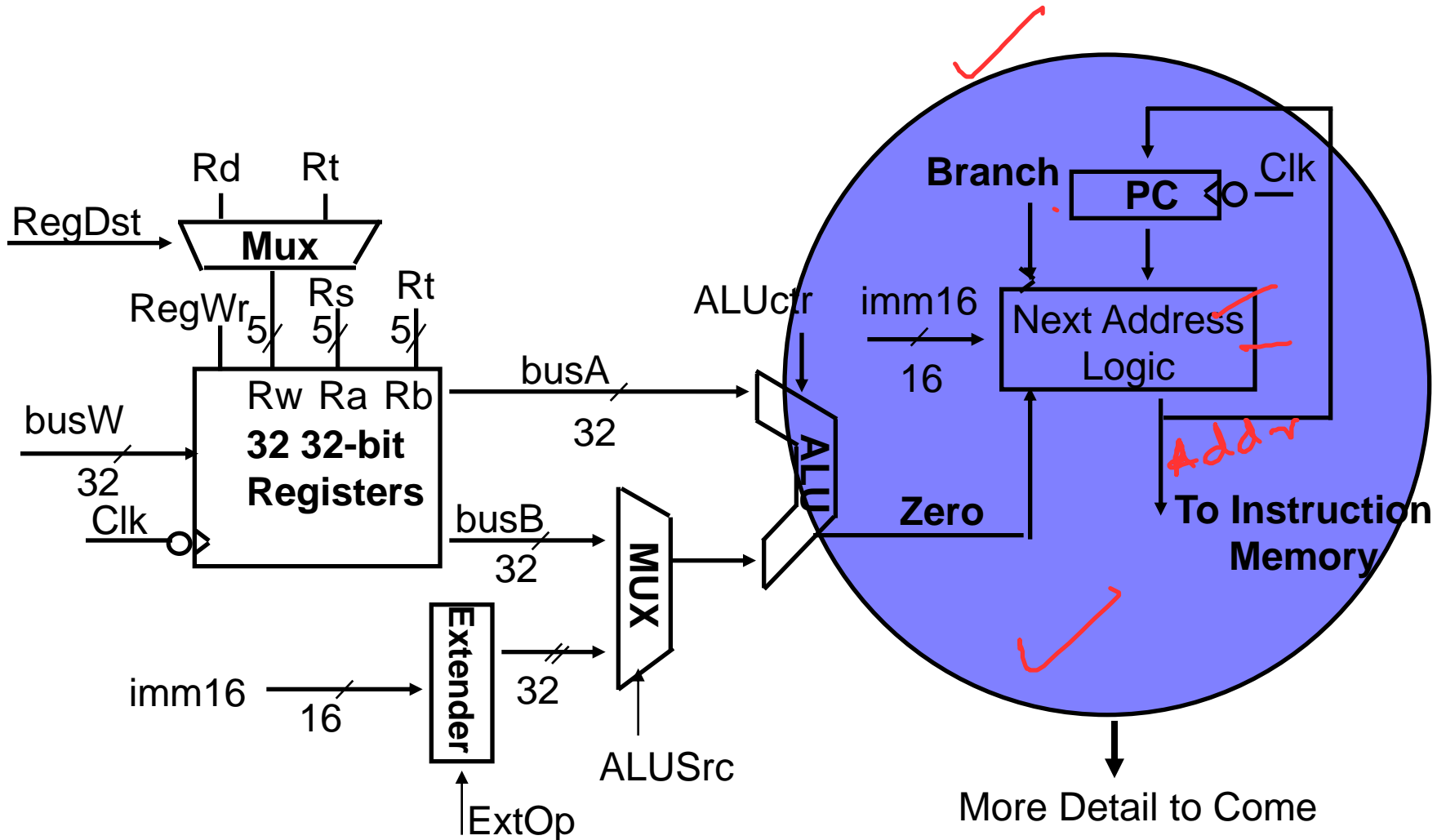

The Next Address

- PC is byte-addressed in instruction memory
 - Sequential

$$\text{PC}[31:0] = \text{PC}[31:0] + 4$$

- Branch operation

$$\text{PC}[31:0] = \text{PC}[31:0] + 4 + \text{SignExt}(\text{imm}) \times 4$$

- Instruction Addresses

- PC is byte addressed, but instructions are 4 bytes long

- Therefore 2 LSBs of the 32 bit PC are always 0

- No reason to have hardware keep the 2 LSBs

⇒ Simplify hardware by using 30 bit PC

- Sequential


$$\text{PC}[31:2] = \text{PC}[31:2] + 1$$

- Branch operation

$$\text{PC}[31:2] = \text{PC}[31:2] + 1 + \text{SignExt}(\text{imm})$$


Datapath: Fast, Expensive Next-IF Logic

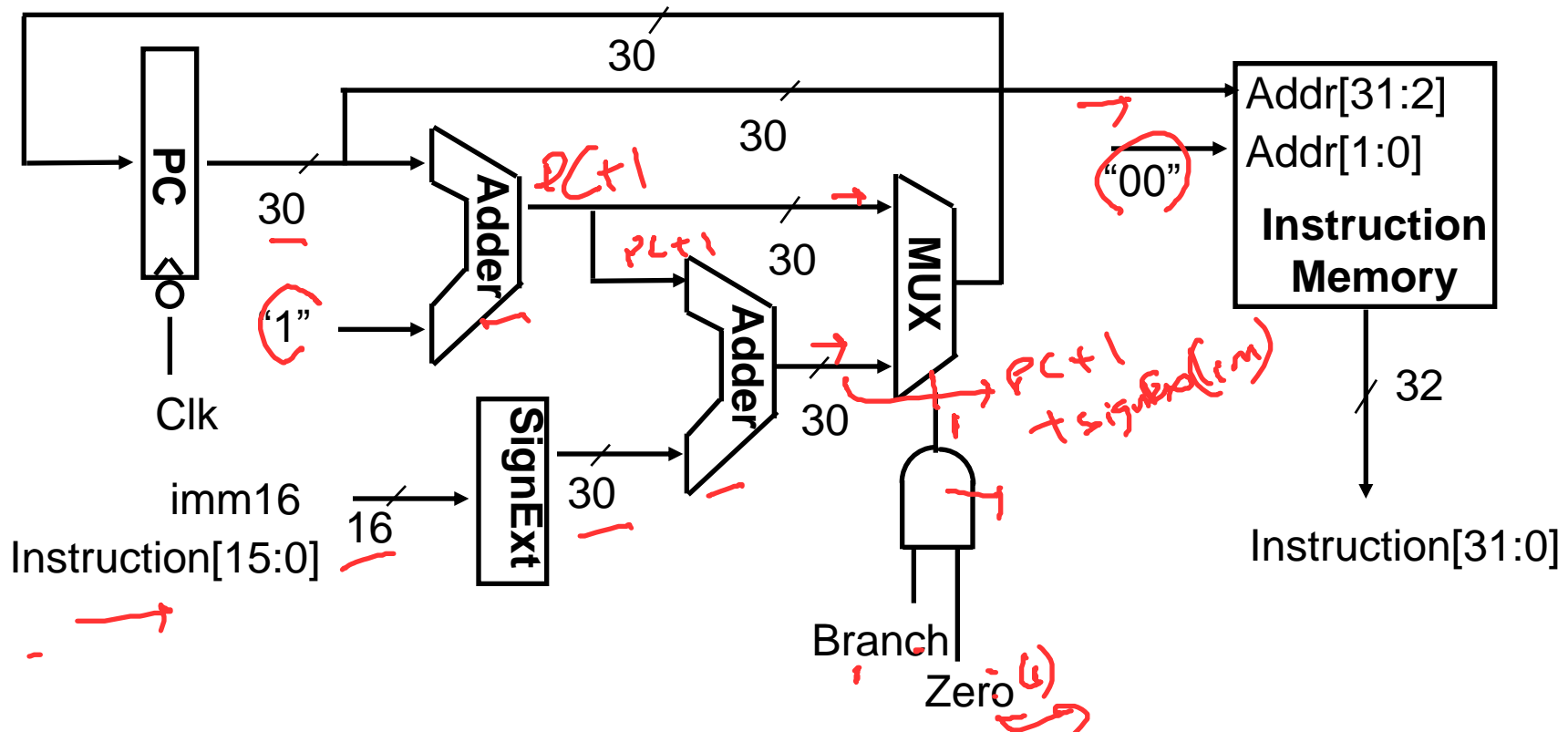- PC incremented to next instruction normally
- On beq instruction then can add immediate $\times 4$ to PC + 4



Datapath: Slow, Smaller Next-IF Logic

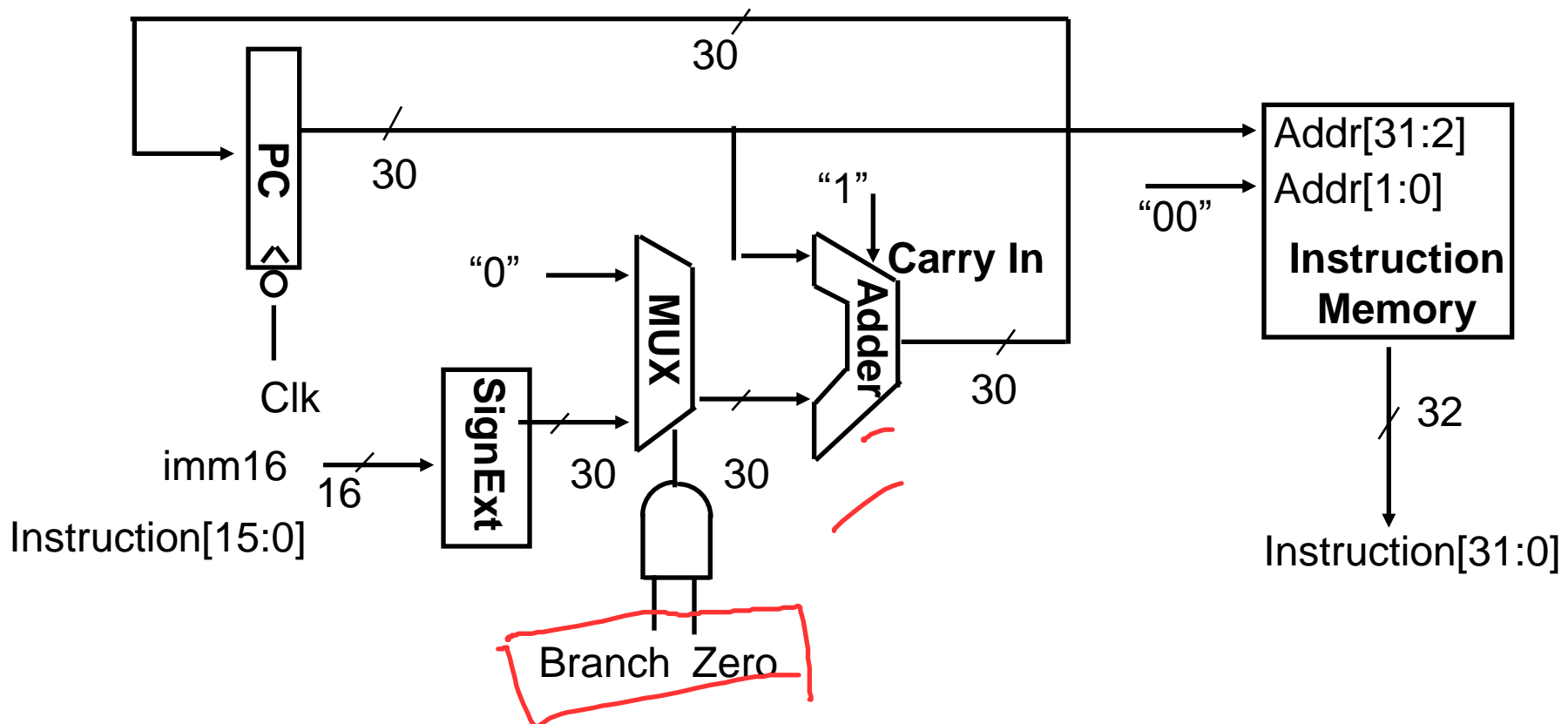- Slow because cannot start address add until ALU zero
- But probably not the critical path (LOAD is usually)



Jump RTL

- Jump instruction

j target

```
Mem[PC];           Fetch instruction from memory
PC[31:2] <- PC[31:28] ||
    target[25:0];    Calculate next address
```

Bits

6


26



jump target address

Datapath: IFU with Jump

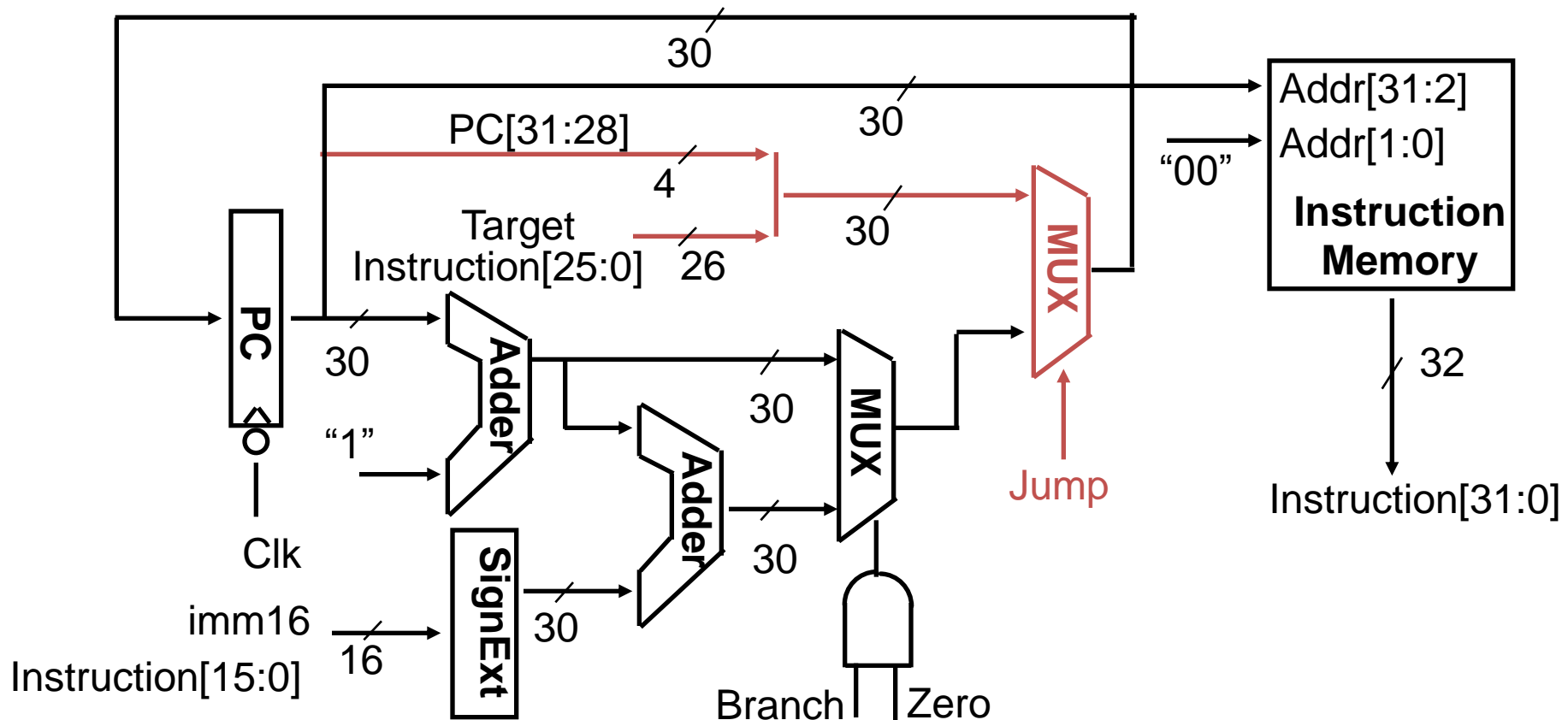- MUX controls if PC is pseudodirect jump



Putting it All Together

